

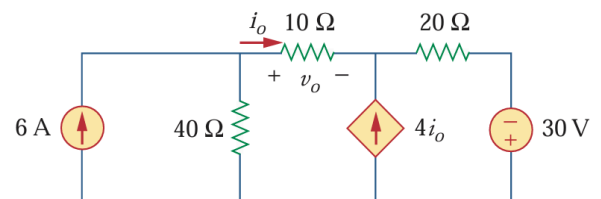
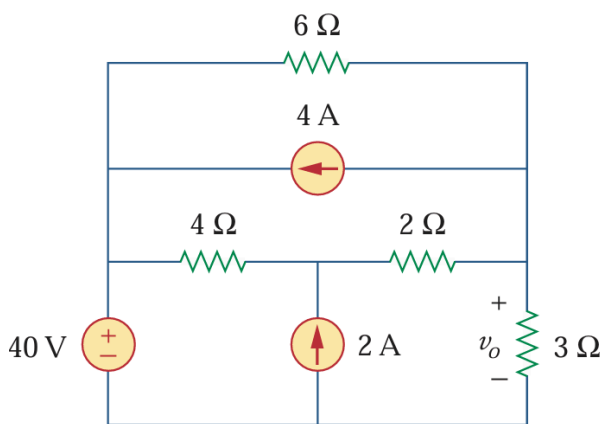
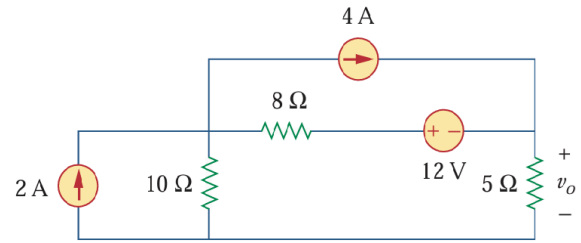
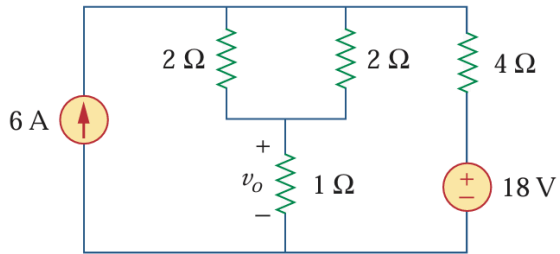
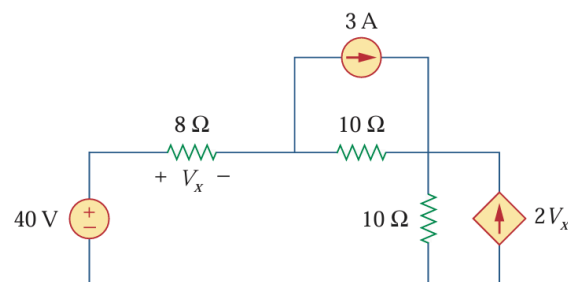
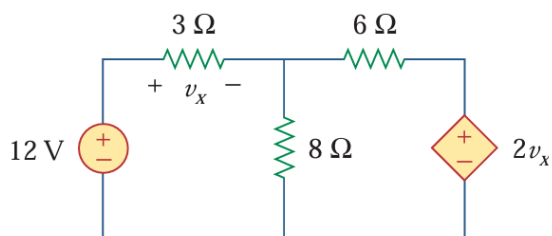


Superposition Theorem:

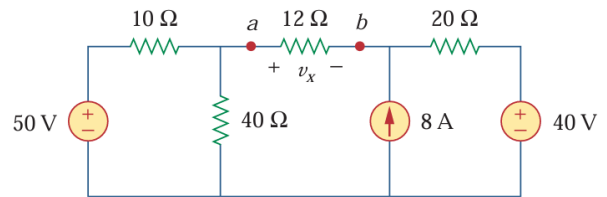


Source Transformation Theorem:

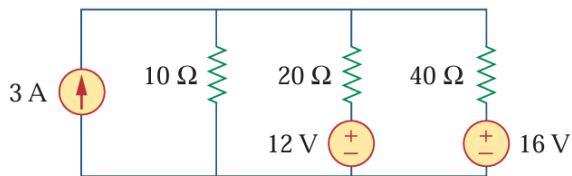Find the current through 10 ohm resistor.




Thevenin's Theorem

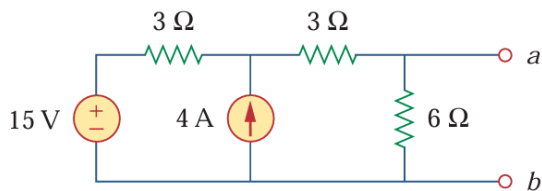
- Find the Thevenin's Equivalent Circuit. (N.B. Load resistance already excluded in the circuit)
- Also find the value of Load resistance for maximum power.



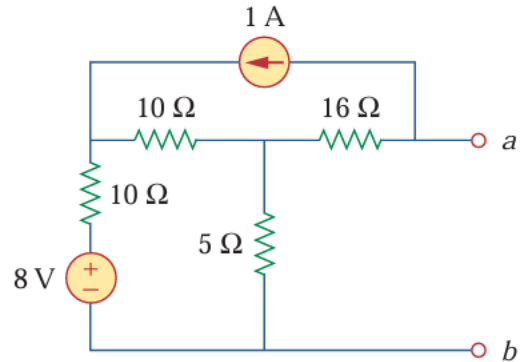- Find the Thevenin's Equivalent Circuit (N.B. Load resistance already excluded in the circuit).
- Also find the value of Load resistance for maximum power.



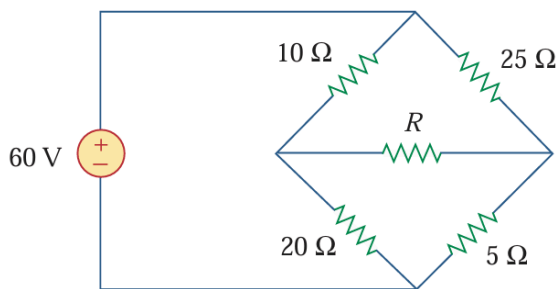Consider R as Load Resistance. Now, Find the Thevenin's Equivalent Circuit and also find the value of Load resistance for maximum power



- Find the Thevenin's Equivalent Circuit

